
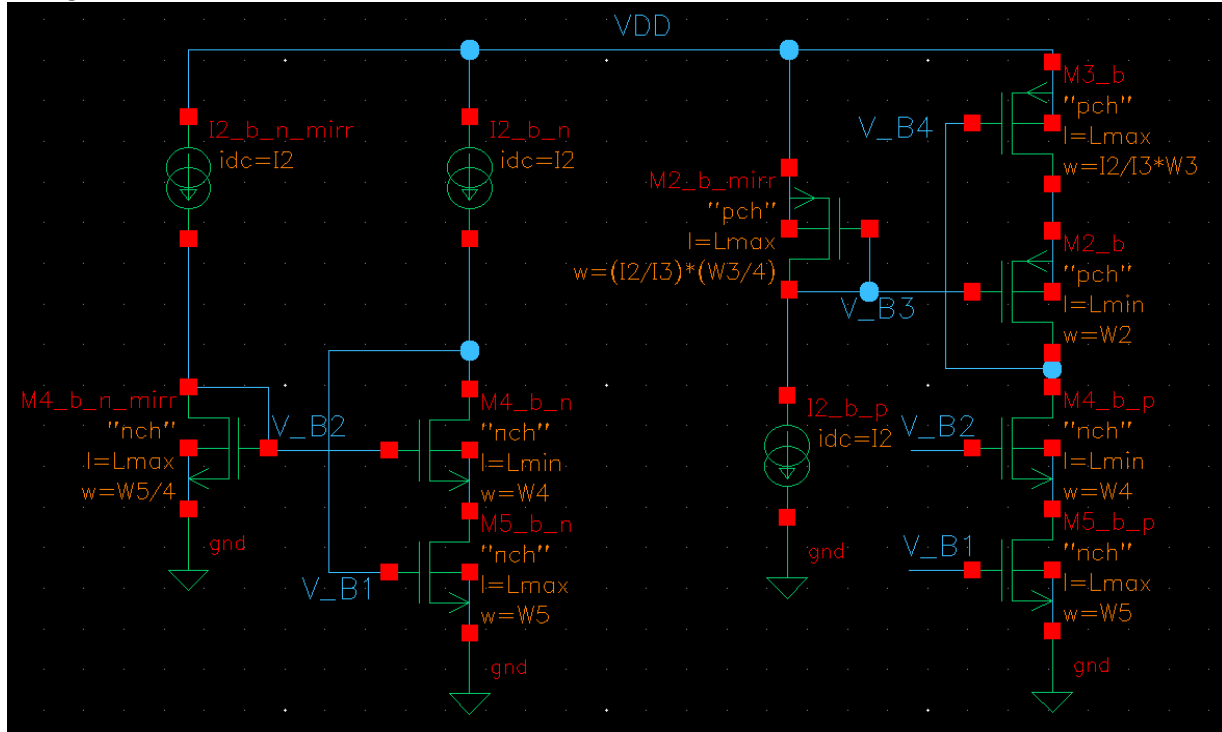


Biasing circuit:

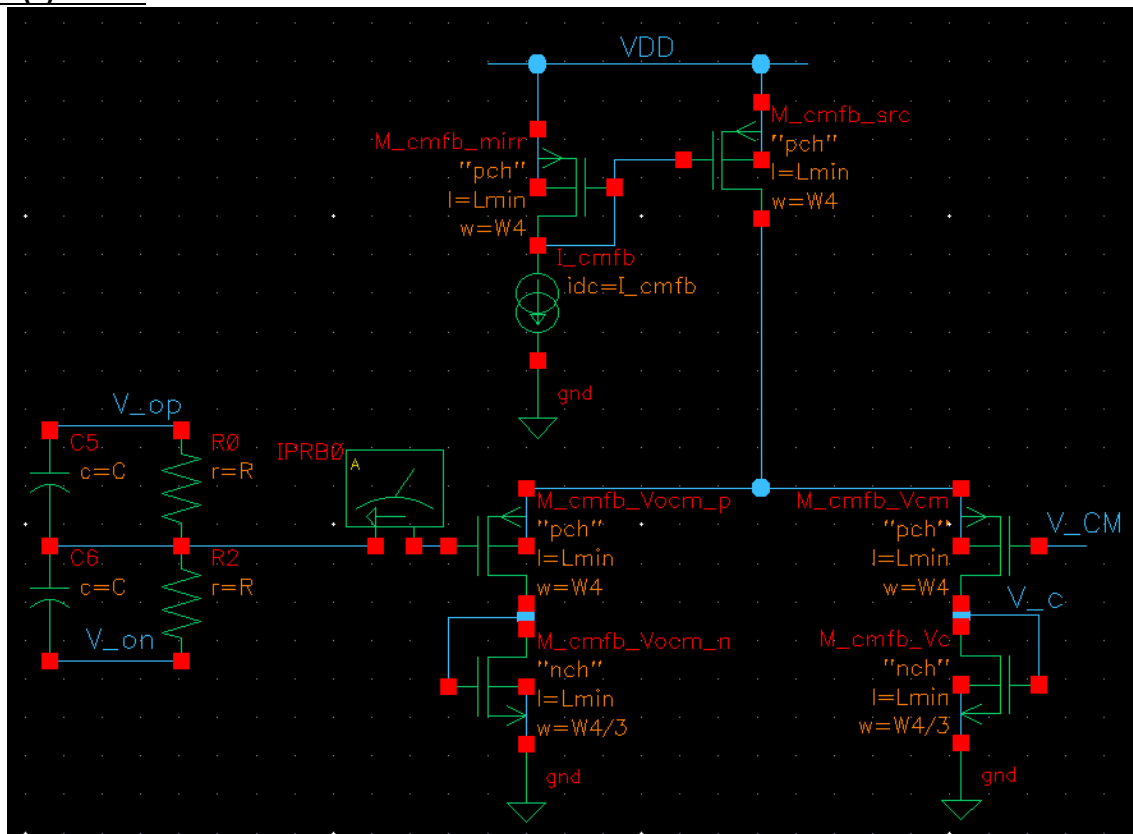

CFMB(3) circuit:



Design Variables:

	Name	Value
1	va	810u
2	I_cmfb	66u
3	I1	220u
4	I2	50u
5	I3	270u
6	W1	36u
7	W2	40u
8	W3	138u
9	W4	12u
10	W5	9u
11	Lmin	180n
12	Lmax	500n
13	R	1M
14	C	15f
15	C_bias	5p
16	VDD	1.8
17	f	10K
18	C_L	5p

Calculations and Analysis

1. Overdrive voltages:

$$\Delta V_{o,pk-pk} = 1.4 \text{ V}$$
$$V_{DD} = 1.8 \text{ V}$$

$$|V_{ov_2}| + |V_{ov_3}| = V_{ov_4} + V_{ov_5} = \frac{V_{DD} - \Delta V_{o,pk-pk}}{2} = \frac{1.8 - 1.4}{2} = 0.2 \text{ V}$$

$$|V_{ov_2}| < |V_{ov_3}| \Rightarrow |V_{ov_2}| = \mathbf{0.05 \text{ V}} \text{ (cascode)} \text{ and } |V_{ov_3}| = 0.2 - 0.05 = \mathbf{0.15 \text{ V}} \text{ (main)} \text{ [assume]}$$

$$V_{ov_4} < V_{ov_5} \Rightarrow V_{ov_4} = \mathbf{0.05 \text{ V}} \text{ (cascode)} \text{ and } V_{ov_5} = 0.2 - 0.05 = \mathbf{0.15 \text{ V}} \text{ (main)} \text{ [assume]}$$

$$V_{ov_1} = |V_{ov_2}| = V_{ov_4} = \mathbf{0.1 \text{ V}} \text{ (input)} \text{ [assume]}$$

2. Device sizes:

$$g_{m_1} \geq 2\pi f_{ugb} C_L = 2\pi(100 * 10^6)(5 * 10^{-9}) \Rightarrow g_{m_1} \geq \mathbf{3.1 \text{ mS}}$$

$$\frac{2I_1}{V_{ov,1}} = g_{m_1} \Rightarrow I_1 = \frac{3.1 * 10^{-3} * 0.1}{2} = 157 \mu\text{A}$$

Let us assume $L_1 = \mathbf{0.18 \mu m}$ (input)

NMOS I_D versus V_{ov} plot: current is $44.73 \mu\text{A}$ for a $10 \mu\text{m}$ wide device at $V_{ov} = 0.05 \text{ V}$

$$W_1 = \left\lceil \frac{157}{44.73} * 10 \right\rceil = \mathbf{36 \mu m}$$

Let us assume $I_2 = I_4 = I_5 = 50\mu A \sim \frac{I_1}{3}$

Let us assume $L_2 = 0.18 \mu m$ (cascode)

PMOS I_D versus V_{ov} plot: current is $12.68 \mu A$ for a $10 \mu m$ wide device at $|V_{ov}| = 0.05 V$

$$W_2 = \left\lceil \frac{50}{12.68} * 10 \right\rceil = 40 \mu m$$

$$I_3 = I_1 + I_2 = 207 \mu A$$

Let us assume $L_3 = 0.25 \mu m$ (main)

PMOS I_D versus V_{ov} plot: current is $37.25 \mu A$ for a $10 \mu m$ wide device at $|V_{ov}| = 0.15 V$

$$W_3 = \left\lceil \frac{207}{37.25} * 10 \right\rceil = 56 \mu m$$

Let us assume $L_4 = 0.18 \mu m$ (cascode)

NMOS I_D versus V_{ov} plot: current is $44.73 \mu A$ for a $10 \mu m$ wide device at $V_{ov} = 0.05 V$

$$W_4 = \left\lceil \frac{50}{44.73} * 10 \right\rceil = 12 \mu m$$

Let us assume $L_5 = 0.25 \mu m$ (main)

NMOS I_D versus V_{ov} plot: current is $131 \mu A$ for a $10 \mu m$ wide device at $V_{ov} = 0.15 V$

$$W_5 = \left\lceil \frac{50}{131} * 10 \right\rceil = 4 \mu m$$

3. CMFB Compensation Parameters & Device Resizing:

For CMFB(3): $f_p = \frac{1}{R'_L C'_L}$ where $R'_L = R || R_L$ and $C'_L = C + C_L$.

Therefore, R should be maximized and C should be minimized.

$R = 1 M\Omega$ and $C = 15 fF$ (assume)

$$\text{Gain of CMFB stage: } A_{o,CMFB} = \frac{g_{m_{CMFB1}}}{g_{m_{CMFB3}}} \sim 3 \text{ (assume)}$$

To achieve this, $L_{CMFB1} = L_{CMFB3}$ and $W_{CMFB1} = 3W_{CMFB3} = W_4$ (assume)

This CMFB design does not give enough f_{ugb} .

To increase f_{ugb} and f_p , we should increase R_L because $C'_L \sim C_L$ which is given.

R_L can be increased by increasing L_3 and L_5 .

Let us assume $L_3 = 0.5 \mu m$ (main)

PMOS I_D versus V_{ov} plot: current is $15.08 \mu A$ for a $10 \mu m$ wide device at $|V_{ov}| = 0.15 V$

$$W_3 = \left\lceil \frac{207}{15.08} * 10 \right\rceil = 138 \mu m$$


Let us assume $L_5 = 0.5 \mu m$ (main)

NMOS I_D versus V_{ov} plot: current is $57.27 \mu A$ for a $10 \mu m$ wide device at $V_{ov} = 0.15 V$


$$W_5 = \left\lceil \frac{50}{57.27} * 10 \right\rceil = 9 \mu m$$

Results


Transient Simulation

 

AC Simulation

 

CMFB Loop Stability

 

Stability Summary - circuit "fd_folded_cascode_cmfb3" with loop probe "IPRB0"			
PM(deg)	@Freq(Hz)	GM(dB)	@Freq(Hz)
73.384	29.39M	28.245	392.14M

Transient Operating Points:

signal	OPT("/M1p" "??")
gm	3.923m

signal	OPT("/M3p" "??")
gm	2.956m

signal	OPT("/M5p" "??")
gm	615.5u

Thermal Noise Analysis:

$$P_{sig} = \frac{V_{peak,FD}^2}{2} = \frac{(1.4 V)^2}{2} = 0.98 V^2$$

From simulations:

$$g_{m_1} = 3.923 mS$$

$$g_{m_3} = 2.956 mS = \frac{2.956}{3.923} g_{m_1} = 0.754 g_{m_1}$$

$$g_{m_5} = 615.5 \mu S = \frac{615.5}{3923} g_{m_1} = 0.157 g_{m_1}$$

$$\Rightarrow g_{m_1} + g_{m_2} + g_{m_3} = g_{m_1} + 0.754 g_{m_1} + 0.157 g_{m_1} = 1.911 g_{m_1}$$

In the presence of biasing capacitors (to attenuate noise from biasing current mirrors):

$$P_{out,n} = \overline{v_{o,n,tot}^2} = \frac{2kT}{C_L} \gamma (g_{m_1} + g_{m_3} + g_{m_5}) R_o = \frac{2kT}{C_L} \gamma \times 1.911 g_{m_1} R_o$$

$$\text{Assume } \gamma = \frac{2}{3}$$

$$\text{From simulations: } |A_{DC}| = 2g_{m_1} R_o = 10^{\frac{59.25}{20}} = 917.28 \Rightarrow g_{m_1} R_o = \frac{917.29}{2} = 458.64$$

$$\begin{aligned} \Rightarrow P_{out,n} &= \frac{2 \times 1.38 \times 10^{-23} m^2 kg s^{-2} K^{-1} \times 300K}{5 \times 10^{-12} F} \times \frac{2}{3} \times 1.911 \times 458.64 \\ &= 96763.41 \times 10^{-11} V^2 \end{aligned}$$

$$SNR = 10 \log_{10} \frac{P_{sig}}{P_{out,n}} = 10 \log_{10} \frac{0.98}{96763.41 \times 10^{-11}} = 10 \log_{10} 1012779.52 = \mathbf{60.055 dB}$$

Summary

<u>Parameter</u>	<u>Specification</u>	<u>Achieved</u>
FD DC Gain	> 400	$10^{\frac{59.25}{20}} = \mathbf{917.28 \checkmark (2x+)}$
Load Cap	5 pF	5 pF ✓
Output FD signal	1.4 V	$0.7038 \times 2 = \mathbf{1.408 V \checkmark}$
VDD	1.8 V	1.8 V ✓
UGB Frequency	100 MHz	103.699 MHz ✓
PM	> 70°	$-96.067^\circ - (-180^\circ) = \mathbf{83.93^\circ \checkmark}$
SNR	> 60 dB	60.055 dB ✓